

Question 1:

Explain the following terms in relation to a measurement system. Given an example for each error.

- a. Static error
- b. Dynamic error
- c. Intrinsic error
- d. Influence error
- e. Systematic error
- f. Random error
- g. Absolute error
- h. Relative error

Question 2:

- a. Explain the term 'loading effect'.
- b. An amplifier with an opamp is used to measure the output of a weak source such as a transducer. Explain what you understand from the term 'weak source'. Would you use an inverting amplifier or a non-inverting amplifier? Justify your answer.
- c. A potentiometric displacement transducer is used to measure the displacement x , where $0 \leq x \leq 1$. The circuit used is shown in Fig.2. Prove that the non-linearity error, $N(x)$, due to the loading of the voltmeter is

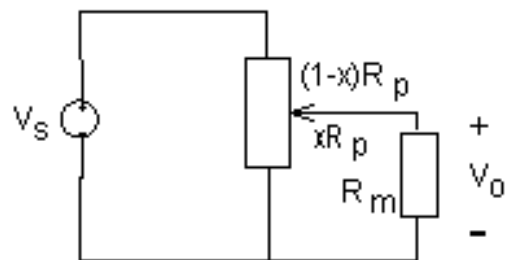


Fig. 2

$$N(x) = V_s \frac{x^2(1-x) \left(\frac{R_p}{R_m} \right)}{1 + x(1-x) \left(\frac{R_p}{R_m} \right)}$$

The resistance of the voltmeter is shown to be R_m . Find the value of x for which $N(x)$ is maximum, assuming $R_p \ll R_m$.

Question 3:

List and describe the static and dynamic characteristics of DAS components.

Question 4:

Describe the following terms with suitable sketches:

- a. Responsivity
 - b. Repeatability
 - c. Backlash
 - d. Nonlinearity
 - e. BSL (how to obtain the coefficients given a set of data)
-

Question 5:

Describe the following terms:

- a. Sensor and transducer (the distinction between them)
 - b. Self-generating transducers with examples
 - c. Modulating transducers with examples
 - d. Doebelin's Generalized input-output model of a transducer
 - e. The differential, ratiometric and feedback measurement structures.
-

Question 6:

- a. Describe the functioning of a piezoelectric transducer.
 - b. Draw the equivalent circuit of a piezoelectric transducer and show how a charge amplifier to measure the output of a piezoelectric transducer.
 - c. Derive the transfer function of the system consisting of the piezoelectric transducer and the charge amplifier.
-

Question 7:

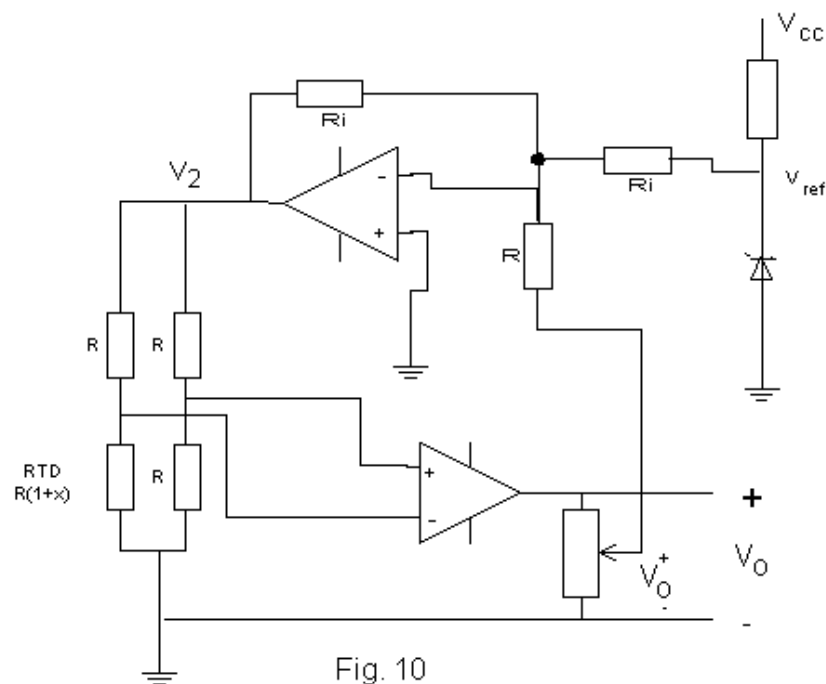
What are the empirical laws of thermocouple circuits ? List the three laws and explain them.

Question 8:

- How can a diode or a bipolar transistor be used as a temperature sensor? Illustrate with suitable diagrams and equations.
- What is a PTAT sensor ? Describe the functioning of AD590 IC temperature sensor.

Question 9:

- Distinguish between photodiodes and photovoltaic cells. Describe how they operate.
- Draw the circuit model of a photodiode in the photovoltaic mode of the operation. Explain the model. What is the open-circuit voltage that can be obtained ? What is the voltage that is delivered to a load resistor if a load resistor is connected across the photovoltaic cell ?
- Draw the circuit model of a photodiode in photocurrent mode. Draw the voltage/current characteristics at different values of irradiance.

Question 10

For the circuit in Fig. 10 prove that

$$\frac{V_o}{V_{ref}} = \frac{AX}{4\left(1 + \frac{x}{2}\right)\left(1 - \frac{A\beta x}{4\left(1 + \frac{x}{2}\right)}\right)}$$

What is the value of β if $V_o = A.V_{ref} \frac{x}{4}$?

Question 11:

Draw the equivalent circuit of a differential inductive pressure transducer. Describe how this transducer functions with the help of phasor diagrams for different unbalanced conditions.

Question 12:

In a system, it is necessary to sample eight analogue signals simultaneously and the values sampled are passed through to a multiplexer and analogue-to-digital converter in turn and the digital outputs from the ADC are collected by a microcontroller system for further processing.

- a. Draw the block diagram of the proposed DAS and explain how the proposed DAS would meet the requirement that the signal are sampled simultaneously.
 - b. Indicate the various delays that can occur in the proposed DAS.
 - c. Assign suitable values to those delays and compute the highest sampling rate per channel of the DAS.
-

Question 13:

Explain the operation of a Delta-Sigma ADC with the help of a block diagram and suitable waveforms.

Question 14:

Explain what is meant by zero-order and first-order reconstruction when an analogue signal is recovered from the output of a DAC.

Question 15:

Explain the following terms:

- Effective Number of bits, ENOB
- Anti-aliasing filter
- Signal-to-Noise Ratio, SNR
- Aperture error for ADC
- Non-Monotonicity

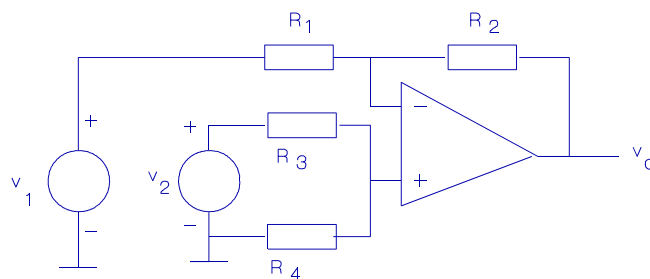
Question 16:

Fig. 16 : Difference Amplifier

For the difference amplifier in Fig. 16, the CMR_R , prove that the common mode rejection determined by the resistance network is given by

$$CMR_R = \frac{1}{2} \times \frac{R_1 R_4 + R_2 R_3 + 2R_2 R_4}{R_1 R_4 - R_2 R_3}$$

Question 17:

An opamp is used as a non-inverting amplifier. The resistance connected between the source and the non-inverting input is 330 k Ω . The gain of the circuit is set to be 10 and the feedback resistor connected between the output and the inverting input terminal is 810 k Ω .

The source voltage is 5 V. The offset voltage of the opamp is 5 μ V. The bias current flowing into the inverting input terminal is 800 nA and the bias current flowing into the non-inverting input terminal is 500 nA. The open-loop gain of the opamp is 10^5 .

- a. Draw the equivalent circuit that includes the bias currents, the offset voltage, the gain of the opamp.
 - b. Obtain the output voltage of the opamp.
 - c. What is the error in percentage due to the non-ideal parameters?
-

Question 18:

Explain the following terms:

- a. Anti-aliasing filter
 - b. Quantisation error
 - c. Aperture time and aperture error
 - d. Reed relay
 - e. Static MUX errors
 - f. Dynamic MUX errors
 - g. Acquisition Time for Sample and Hold circuit
 - h. Differential non-linearity for DAC
 - i. ENOB
 - j. THD
 - k. Glitch in relation to a DAC
-

Question 19:

Given that the signal fed to ADC is a sinusoidal signal and the number of bits of conversion is n , derive an expression for the signal-to-noise ratio, SNR. Illustrate your answer with the help of suitable diagrams.

Question 20:

How is the digital output of ADC coded? Specify the popular codes used and show how they represent the output.

Question 21:

Draw the circuit of a 6-bit R-2R ladder DAC and explain its working.

Question 22:

Draw the circuit diagram of a 4-bit flash ADC and explain its working. How does an ADC with pipeline architecture work ?

Question 23:

Draw the block diagram of a typical DAS. List the common dc and ac errors. Show how you would work out an error budget.
